

## OHM'S LAW

*The rate of the flow of the current is equal to electromotive force divided by resistance.*

**I = Intensity of Current = Amperes**

**E = Electromotive Force = Volts**

**R = Resistance = Ohms**

**P = Power = Watts**


The three basic Ohm's law formulas are:

$$I = \frac{E}{R}$$

$$R = \frac{E}{I}$$

$$E = I \times R$$

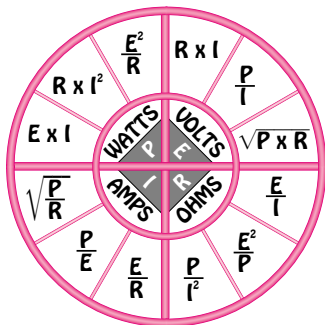Below is a chart containing the formulas related to Ohm's law. To use the chart, from the center circle, select the value you need to find, I (Amps), R (Ohms), E (Volts) or P (Watts). Then select the formula containing the values you know from the corresponding chart quadrant.



Example:

An electric appliance is rated at 1200 Watts, and is connected to 120 Volts. How much current will it draw?

$$\text{Amperes} = \frac{\text{Watts}}{\text{Volts}} \quad I = \frac{P}{E} \quad I = \frac{1200}{120} = 10 \text{ A}$$

What is the Resistance of the same appliance?

$$\text{Ohms} = \frac{\text{Volts}}{\text{Amperes}} \quad R = \frac{E}{I} \quad R = \frac{120}{10} = 12 \Omega$$

## OHM'S LAW

In the preceding example, we know the following values:

$$I = \text{amps} = 10$$

$$R = \text{ohms} = 12\Omega$$

$$E = \text{volts} = 120$$

$$P = \text{watts} = 1200$$

We can now see how the twelve formulas in the Ohm's Law chart can be applied.

$$\text{AMPS} = \sqrt{\frac{\text{WATTS}}{\text{OHMS}}} \quad I = \sqrt{\frac{P}{R}} = \sqrt{\frac{1200}{12}} = \sqrt{100} = 10A$$

$$\text{AMPS} = \frac{\text{VOLTS}}{\text{OHMS}} \quad I = \frac{P}{E} = \frac{1200}{120} = 10A$$

$$\text{AMPS} = \frac{\text{VOLTS}}{\text{OHMS}} \quad I = \frac{E}{R} = \frac{120}{12} = 10A$$

---

$$\text{WATTS} = \frac{\text{VOLTS}^2}{\text{OHMS}} \quad P = \frac{E^2}{R} = \frac{120^2}{12} = \frac{14,400}{12} = 1200W$$

$$\text{WATTS} = \text{VOLTS} \times \text{AMPS} \quad P = E \times I = 120 \times 10 = 1200W$$

$$\text{WATTS} = \text{AMPS}^2 \times \text{OHMS} \quad P = I^2 \times R = 100 \times 12 = 1200W$$

---

$$\text{VOLTS} = \sqrt{\text{WATTS} \times \text{OHMS}} \quad E = \sqrt{P \times R} = \sqrt{1200 \times 12} = \sqrt{14,400} = 120V$$

$$\text{VOLTS} = \text{AMPS} \times \text{OHMS} \quad E = I \times R = 10 \times 12 = 120V$$

$$\text{VOLTS} = \frac{\text{WATTS}}{\text{AMPS}} \quad E = \frac{P}{I} = \frac{1200}{10} = 120V$$

---

$$\text{OHMS} = \frac{\text{VOLTS}^2}{\text{WATTS}} \quad R = \frac{E^2}{P} = \frac{120^2}{1,200} = \frac{14,400}{1,200} = 12\Omega$$

$$\text{OHMS} = \frac{\text{WATTS}}{\text{AMPS}^2} \quad R = \frac{P}{I^2} = \frac{1200}{100} = 12\Omega$$

$$\text{OHMS} = \frac{\text{VOLTS}}{\text{AMPS}} \quad R = \frac{E}{I} = \frac{120}{10} = 12\Omega$$